

Quiz - 2

Due Feb 25 at 11:59pm

Points 100

Questions 25

Time Limit None

Allowed Attempts Unlimited

[Take the Quiz Again](#)

Attempt History

	Attempt	Time	Score
KEPT	Attempt 6	3 minutes	100 out of 100
LATEST	Attempt 6	3 minutes	100 out of 100
	Attempt 5	2 minutes	96 out of 100
	Attempt 4	6 minutes	92 out of 100
	Attempt 3	22 minutes	88 out of 100
	Attempt 2	23 minutes	64 out of 100
	Attempt 1	72 minutes	52 out of 100

! Correct answers are hidden.

Score for this attempt: **100** out of 100

Submitted Feb 24 at 11:10pm

This attempt took 3 minutes.

Question 1

4 / 4 pts

When a voltage of 0V (Low) is applied to the Gate of a PMOS transistor, the transistor is:

- ☐ OFF
- ☐ Not enough information
- ☒ ON

Question 2

4 / 4 pts

Tri-state inverter gate has:

- ☐ 2 NMOS transistors in the Pull Up Network

- ☐ 2 PMOS transistors in the Pull-Down Network
- ☒ 2 NMOS transistors in series and 2 PMOS transistors in series
- ☐ 2 NMOS transistors in series and 2 PMOS transistors in parallel

Question 3**4 / 4 pts**

The amount of drain current (I_{DS}) depends on:

- 1) Gate to Source voltage (V_{GS})
- 2) Drain to Source voltage (V_{DS})
- 3) Bulk to Source voltage (V_{SB})
- 4) Threshold voltage (V_{th})
- 5) Dimensions of MOSFET (W/L)

- ☐ Only 1st, 2nd and 3rd options
- ☒ All of the mentioned
- ☐ Only 1st option
- ☐ Only 5th option

Question 4**4 / 4 pts**

When a voltage of 0V (Low) is applied to the Gate of an NMOS transistor, the transistor is:

- ☐ Not enough information
- ☒ OFF
- ☐ ON

Question 5**4 / 4 pts**

Which of the following will reduce the power dissipated by a CMOS inverter?

- ☒ Decrease the supply voltage

- ☐ Increase how often it switches
- ☐ Increase the MOSFET's "off current"
- ☐ None of these
- ☐ Increase the load capacitance

Question 6**4 / 4 pts**

The drain current I_{DS}

- ☐ Depends inversely on $(V_{GS} - V_{th})$ in the triode region
- ☐ None of the mentioned
- ☐ Depends linearly on $(V_{GS} - V_{th})$ in the saturation region
- ☒ Depends on the square of $(V_{GS} - V_{th})$ in the saturation region

Question 7**4 / 4 pts**

When V_{GS} reaches to threshold voltage drain current is:

- ☐ min
- ☐ 10 milli Amps
- ☐ max
- ☒ close to 0

Question 8**4 / 4 pts**

In the Cadence assignments, what tool is used in the DRC and LVS steps of Layout Design.

- ☐ Quantus

☐ Diva☐ Spectre☒ Assura**Question 9****4 / 4 pts**

When the threshold voltage is more, the (sub threshold) leakage current will be

☐ more☒ less

Increasing the threshold voltage, leads to small leakage current when turned off and reduces current flow when turned on.

☐ not enough information to determine☐ none of the mentioned**Question 10****4 / 4 pts**

CMOS inverter transfer curve has _____ regions of operation

☐ three☐ four☐ two☒ five**Question 11****4 / 4 pts**

A MOSFET biased in saturation, can act as a good:

- ☐ inverter
- ☐ buffer
- ☒ current source
- ☐ voltage source

Question 12**4 / 4 pts**

A 2:1 MUX is implemented using transmission gates. How many PMOS transistors does it use?
_____.

- ☐ 1
- ☐ 4
- ☒ 3
- ☐ 5

Question 13**4 / 4 pts**

Because of short channel effect, the _____ of a MOSFET increases with increasing values of L . (Hint: I_{ds} decreases).

- ☐ L
- ☐ mobility
- ☐ W
- ☒ V_{th}

Question 14**4 / 4 pts**

When a voltage of 2V is applied between the G and S of an NMOS, the transistor is: (assume $V_t = 1$ V)

- ☐ Not enough information

☐ OFF☒ ON**Question 15****4 / 4 pts**

When a voltage of -2V is applied to between the G and S of a PMOS transistor, the transistor is (Assume $|V_{tp}| = 1V$):

☐ Not enough information☒ ON☐ OFF**Question 16****4 / 4 pts**

Pick the most appropriate statement from below. A 3-input NOR gate has:

☐ (d) 3 NMOS transistors in series and 3 PMOS transistors in parallel☐ (b) 3 PMOS transistors in the Pull-Down Network☒ (e) Both (a) and (c) are true☐ (c) 3 NMOS transistors in parallel and 3 PMOS transistors in series☐ (a) 3 NMOS transistors in the Pull-Down Network☐ (f) Both (b) and (d) are true**Question 17****4 / 4 pts**

Which of the following is true about PMOS transistor?

☒ It provides a good '1'☐ It uses p-well

- ☐ It provides a good '0'
- ☐ It has positive threshold voltage V_{tp}

Question 18**4 / 4 pts**

Input dependent phase shift is brought about by which of the following transistor non-idealities?

- ☒ Non-zero ON-resistance
- ☐ Channel-charge injection
- ☐ Negative-bias Temperature Instability (NBTI)
- ☐ Clock-feed through

Question 19**4 / 4 pts**

Which of the following Capacitances is fundamental to the operation of a MOS transistor?

- ☒ Oxide Capacitance between Gate and Channel
- ☐ Depletion capacitance between Drain and Bulk
- ☐ Overlap Capacitance between Gate and Source/Drain
- ☐ Depletion capacitance between Source and Bulk

Question 20**4 / 4 pts**

In Figure – 1 shown below, which capacitance shorts the input to the output at high frequencies?

 


Figure – 1. MOSFET Capacitances

- ☐ Csb
- ☐ Cdb
- ☐ Cgs
- ☒ Cgd

Question 21

4 / 4 pts

Shown below are transistor higher-order effects. Identify a lateral field effect from below.

- ☐ c. Body effect
- ☐ b. Mobility degradation
- ☒ d. Velocity saturation
- ☐ a. Subthreshold conduction

Question 22

4 / 4 pts

Shown below are transistor higher-order effects. Identify a vertical field effect from below.

- ☒ b. Mobility degradation
- ☐ d. Velocity saturation
- ☐ c. Body effect
- ☐ a. Subthreshold conduction

Question 23**4 / 4 pts**

"Pinch-off" occurs in which region of operation?

- ☒ Saturation
- ☐ Subthreshold
- ☐ Linear
- ☐ All the regions

Question 24**4 / 4 pts**

By definition, the time from input to rising output crossing $V_{DD}/2$ is:

- ☐ Rising Contamination delay (t_{cdr})
- ☐ Setup – time
- ☐ Rise Time - (t_r)
- ☒ Rising Propagation Delay (t_{pdr})

Question 25**4 / 4 pts**

Which of the following effects will cause current through a MOSFET to be higher than expected?

- ☐ None of these
- ☐ Velocity saturation
- ☒ Drain induced barrier lowering
- ☐ Body effect
- ☐ Mobility degradation

Quiz Score: **100** out of 100