



MARIO PALACIOS

LAB COURSE (CpE 64) SECTION #20

WENDESDAY

INSTRUCTOR: EMMANUEL DUPART

**PART 1. ADDER WITH CONSTANT****Description:**

The objective of this part of the lab is to practice designing more combinational logic circuits and get more experience with equations, K-maps, and Boolean Algebra.

**Problem Description:**

Design a four-bit adder that accepts any 4-bit input and adds a 4-bit binary constant to the input. Create truth tables, use K-maps to find equations and create a circuit schematic diagram. There should be a total of five equations for the five outputs of the adder. Use DeMorgan's theorem and circuit sharing between outputs. When creating schematic design in Multisim use the 4 gates available and the six inverter ICs. Record the outputs in a truth table.


**Engineering Data:**

INPUTS				ADDER OUTPUTS				
A	B	C	D	Sum4	Sum3	Sum2	Sum1	Sum0
0	0	0	0	0	0	1	1	1
0	0	0	1	0	1	0	0	0
0	0	1	0	0	1	0	0	1
0	0	1	1	0	1	0	1	0
0	1	0	0	0	1	0	1	1
0	1	0	1	0	1	1	0	0
0	1	1	0	0	1	1	0	1
0	1	1	1	0	1	1	1	0
1	0	0	0	1	1	1	1	1
1	0	0	1	1	0	0	0	0
1	0	1	0	1	0	0	0	1
1	0	1	1	1	0	0	1	0
1	1	0	0	1	0	0	1	1
1	1	0	1	1	0	1	0	0
1	1	1	0	1	0	1	0	1
1	1	1	1	1	0	1	1	0

**Figure 1. Truth Table for ADDER with CONSTANT (0111)[7]**

Red	Blue	Purple	Green	Black
$A$	$\bar{A}(D + C + B) + A\bar{B}\bar{C}\bar{D}$	$B(D + C) + \bar{B}\bar{C}\bar{D}$	$\bar{C}\bar{D} + CD$	$\bar{D}$

**Figure 2. Simplified Boolean Expressions**

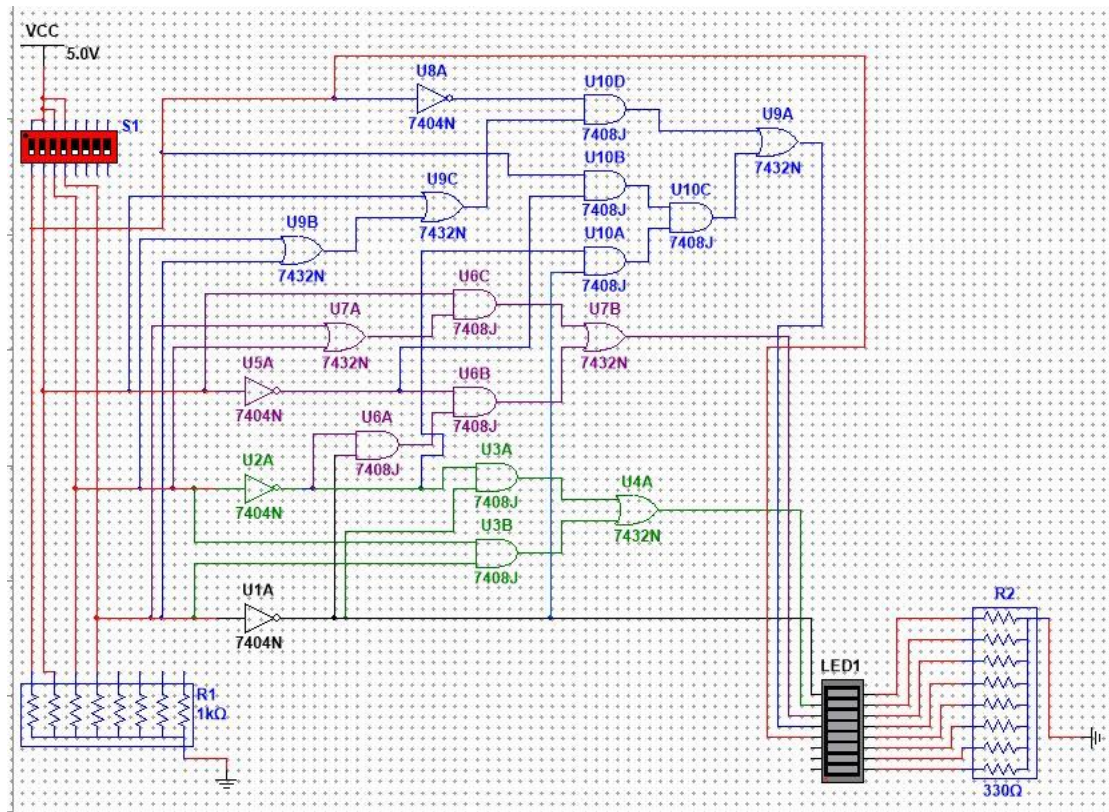

**Figure 3. Circuit Schematic for 5 Boolean Equations**

### Conclusion:

In conclusion creating an adder is possible if a K-map is made from which a truth table is needed. This part was great for practicing my skills for combinational logic. This part of the lab took me about fifteen minutes to complete.

## PART 2. ADDER WITH CONSTANT CONTINUED

### Description:

The object of this part is to practice Verilog writing techniques and testbench creating knowledge.

### Problem Description:

Using the five Boolean equations created in the previous part write a Data Flow model description in Verilog HDL. Then test the Verilog solution on the FPGA board. Create a testbench and see if the waveform matches with the predicted results done in the previous part.

**Engineering Data:**


The Boolean equations that were derived from the truth table and K-maps can be seen on Figure 2 in the first part.

```

1  module part02 (A,B,C,D,sum0,sum1,sum2,sum3,sum4);
2      input A,B,C,D;
3      output sum4,sum3,sum2,sum1,sum0;
4
5      //Red
6      assign sum4 = A;
7
8      //Blue
9      assign sum3 = ~A & ((D|C)|B) | ((A&~B)&(~C&~D));
10
11     //Purple
12     assign sum2 = B & (D|C) | ((~B&~C)&~D);
13
14     //Green
15     assign sum1 = (~C&~D) | (C&D);
16
17     //Black
18     assign sum0 = ~D;
19 endmodule

```

**Figure 4. Verilog in Data Flow Description for Boolean Equations**

 

**Figure 5. Waveform from Boolean Equations**

**Conclusion:**

Overall refining my skills in writing Verilog in Data Flow description allowed me to create short and precise code. This part took me about fifteen minutes to complete

### PART 3. FULL 4-BIT ADDER

#### Description:

To create a full 4-bit adder that adds any 4 bits to any other 4 bits.

#### Problem Description:

Have the two 4-bit numbers be interpreted as unassigned, and call the two numbers A and B. The bits under A will be called a3, a2, a1, and a0; same goes for the bits under B b3, b2, b1, and b0. The adder will have five outputs called s4, s3, s2, s1, s0.

#### Engineering Data:

```

1 module fullAdder(a3,a2,a1,a0,b3,b2,b1,b0,c_out,s3,s2,s1,s0);
2     input a3,a2,a1,a0,b3,b2,b1,b0;
3     output c_out,s3,s2,s1,s0;
4
5     assign {c_out,s3,s2,s1,s0} = {a3,a2,a1,a0}+{b3,b2,b1,b0};
6 endmodule

```

Figure 6. Verilog Code for Full 4-Bit Adder in Structural Modeling

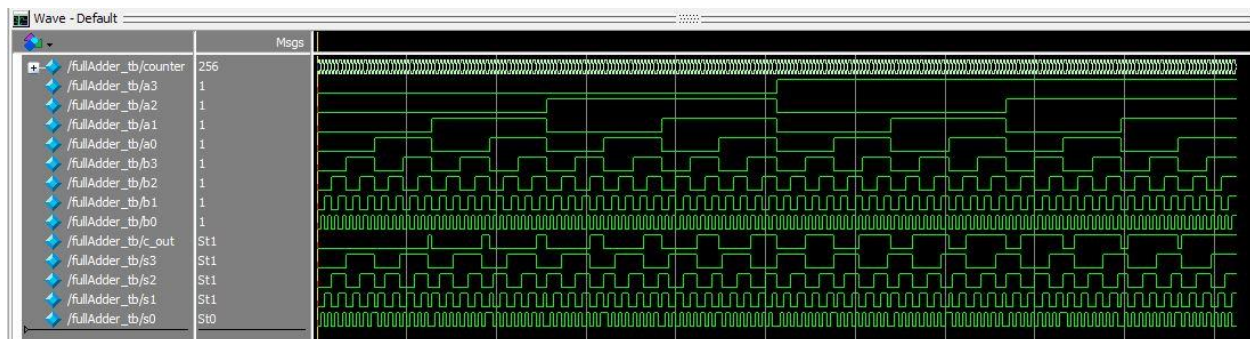


Figure 7. Waveform for 4-Bit Adder

#### Conclusion:

In conclusion the 4-Bit adder allowed me to visualize how this can play a big role in ALUs. I was able to practice more on my Structural modeling for code in Verilog. Overall this part of the lab took me about 15 minutes to complete because it was a continuation of the previous section.



## PART 4. COMPARATOR USING GATES

### Description:

To design a simple combinational circuit, 2-bit comparator, and to gain insight into IC chip minimization instead of gate minimization in implementing the combinational circuit.

### Problem Description:

Create a 4-input, 3-output that compares 2-bit unsigned numbers. Call the 4-inputs a1, a0, b1, and b0; where the most significant bit will be a1/b1 and the least significant a0/b0. We are doing this because it compares the binary number a1a0 with the binary number b1b0. Afterwards draw a circuit diagram with only NAND gates on Multisim.

### Engineering Data:

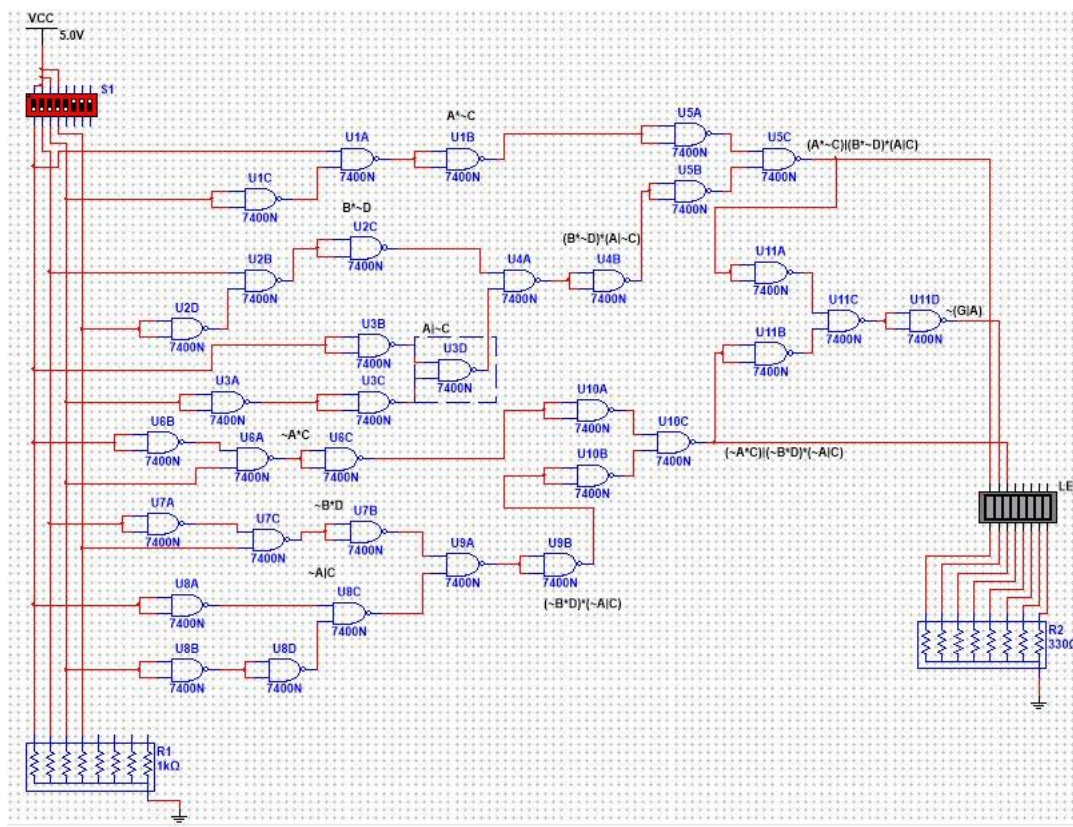


Figure 8. Multisim of NAND Comparator

 


Figure 9. Waveform for Comparator

```

1 module comparator(a0,a1,b0,b1,G,E,L);
2     input a0,a1,b0,b1;
3     output G,E,L;
4     reg G,E,L;
5
6     always@(a0 or a1 or b0 or b1)
7     begin
8         //Less Than
9         L<={a1,a0}<{b1,b0};
10        //Greater Than
11        if ({a1,a0}>{b1,b0})
12            G<=1;
13        else
14            G<=0;
15        //Equivalent To
16        E<={a1,a0}=={b1,b0};
17    end
18 endmodule

```

Figure 10. Verilog for Comparator in “Behavioral” Modeling

**Conclusion:**

The 2-bit comparator takes in two bits and compares them with one another, then it separates which two bits are greater, less than, or equal. A comparator is the important building block for CPUs and microcontrollers. This part of the lab took me about 30 minutes to complete, but afterwards I came out with new found knowledge.