



MARIO PALACIOS

LAB COURSE (CpE 64) SECTION #20

WENDESDAY

INSTRUCTOR: EMMANUEL DUPART

## PART 1. BOOLEAN LOGIC STATE MACHINE

### Description:

Use D Flip-Flops to create a state machine solution for the diagram below (Figure 1). Use K-maps to find equations for each of the inputs.

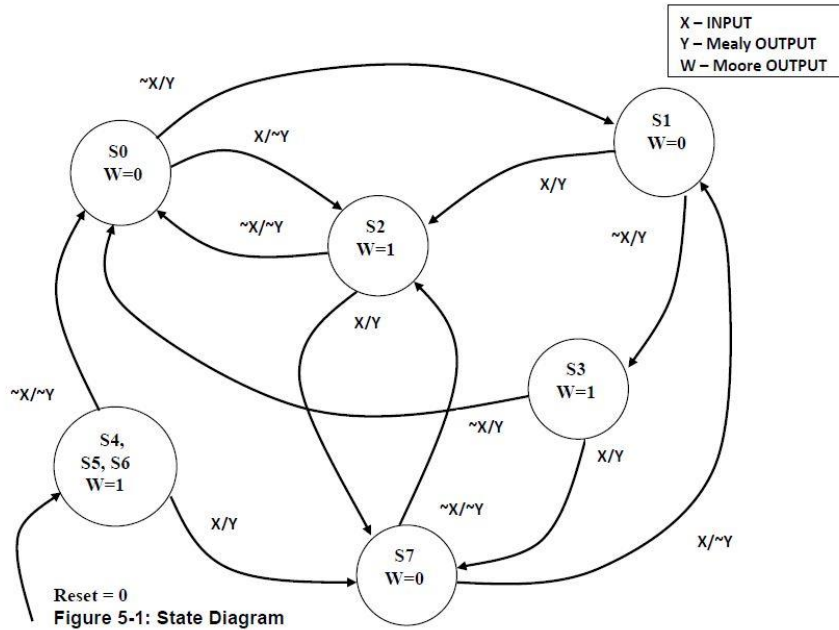


Figure 1. State Machine Diagram

### Problem Description:

Implement the four equations from the K-Maps into Verilog code, following the Data Flow modeling. Since this type of state machine has an “implied” system clock, a clock must be provide for testing.


### Engineering Data:

```


1  module Part1(X,clk,reset,Y,W,CS);
2
3      input X,clk,reset;
4
5      output reg [2:0]CS;
6      output wire Y,W;
7
8      wire NS2,NS1,NS0;
9
10     assign NS2 = (CS[2] | CS[1]) & (~CS[2] | ~CS[1] | ~CS[0]) & X;
11     assign NS1 = X & (~CS[2] | ~CS[1] | ~CS[0]) | CS[0] & ((~CS[2] & ~CS[1]) | (CS[2] & CS[1] & CS[0]));
12     assign NS0 = X & (CS[1] | CS[2]) | (~CS[2] & ~CS[1] & ~X);
13     assign Y = ~CS[2] & (CS[0] | (~CS[1] & ~X)) | X & ((CS[1] & ~CS[0]) | (CS[2] & ~CS[1]));
14     assign W = ((CS[2] & ~CS[1]) | (~CS[2] & CS[1]) | (CS[1] & ~CS[0]));
15
16     always@ (posedge clk) begin
17         if (!reset)
18             CS <= 3'b100;
19         else if (reset)
20             CS <= {NS2,NS1,NS0};
21     end
22 endmodule

```

Figure 2. Verilog Code of Equations in Data Flow

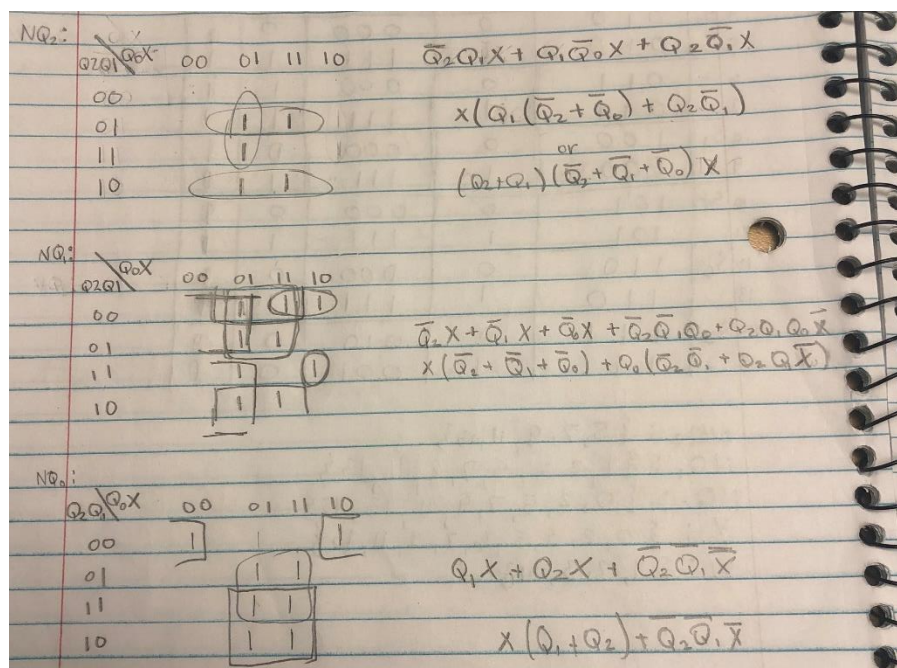

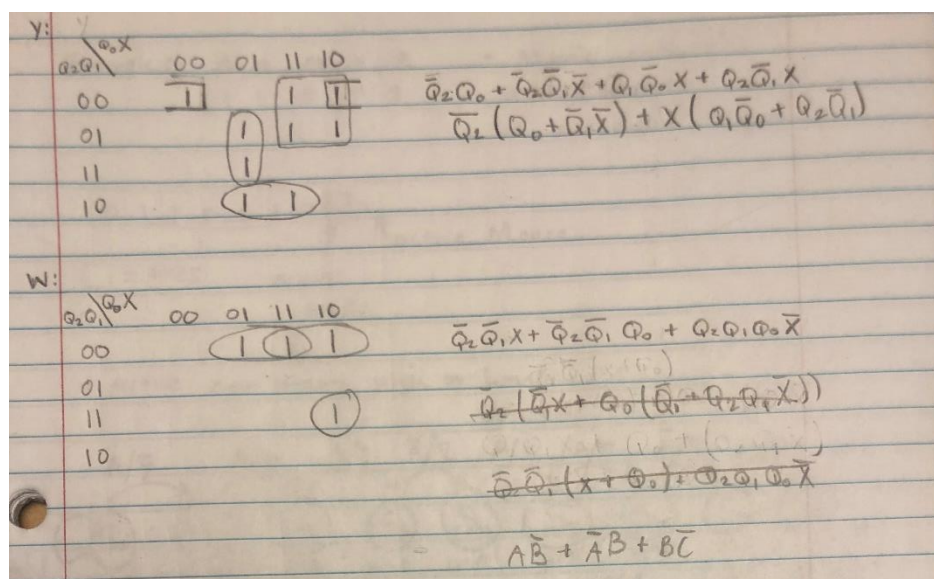
### Figure 3. K-Map Displaying How Equations Were Derived



### Figure 4. K-Map Displaying How Equations Were Derived

When deriving the equations it was important to keep track of the current state and how the input changes the state. There was a total of five equations to implement.

 

**Figure 5. Waveform for State Machine Created Through Equations**

### Conclusion:

In conclusion to determine how many D Flip-Flops will be needed, depends on the amount of states there are present. In this case there were six states present and two to the power of three is seven; meaning there must be at least three D Flip-Flops in order for this state machine to operate properly. This part of the lab took me about an hour to complete because I knew nothing about State Machines. However at the end I knew a good start is to create a truth table and from there get equations through K-Maps.

## PART 2. STATE MACHINE USING BEHAVIORAL MODELING

### Description:

Use Verilog Behavioral Modeling to implement the State Machine in figure 1.

### Problem Description:

Behavioral Modeling means the use of “if else” or “case” statements. Afterwards determine the advantage of writing the description using this method over the other.

### Engineering Data:



**Figure 6. Waveform of State Machine Going Through All Possible States**

When writing the Verilog Code States four, five and six all are in the same state, so I decided to remove it from the code itself.

```

module Part2(clk,reset,x,y,w,current_state);

input wire x,reset,clk;
output reg [1:0] y;
output wire w;

output reg [2:0] current_state;
reg [2:0] next_state;

parameter s0 = 3'b000,
s1 = 3'b001,
s2 = 3'b010,
s3 = 3'b011,
s4 = 3'b100,
s5 = 3'b101,
s6 = 3'b110,
s7 = 3'b111;

always@(posedge clk) begin
current_state <= next_state;
end

assign w = (current_state == s2) | (current_state == s3)
| (current_state == s4) | (current_state == s5) |
(current_state == s6);

/*Default is state 4 b/c reset = 0 and there is
*multiple ones so we skipping state 5 & 6 */
always@(current_state or x) begin
    case(current_state)
        s0: if(x) begin
                                next_state <= s2;
                                y = 0;
                            end
                            else if(!x) begin
                                next_state <= s1;
                                y = 1;
                            end
    endcase
end

s1: if(x) begin
    next_state <= s2;
    y = 1;
end
else if(!x) begin
    next_state <= s3;
    y = 1;
end

s2: if(x) begin
    next_state <= s7;
    y = 1;
end
else if(!x) begin
    next_state <= s0;
    y = 0;
end

s3: if(x) begin
    next_state <= s7;
    y = 1;
end
else if(!x) begin
    next_state <= s0;
    y = 1;
end

s4: if(x) begin
    next_state <= s7;
    y = 1;
end
else if(!x) begin
    next_state <= s0;
    y = 0;
end

s7: if(x) begin
    next_state <= s1;
    y = 0;
end
else if(!x) begin
    next_state <= s2;
    y = 0;
end

default:
    next_state <= s4;
endcase
end
endmodule

```

**Figure 7. Verilog in Behavioral Modeling on Both Text Boxes (Left and Right)**

**Conclusion:**

In conclusion writing Verilog in Behavioral Modeling is a lot faster because, the amount of time spent on the creating the truth table and deriving the equations using K-maps took longer than using “if else” and case statements. This part of the lab took me about 45 minutes because of getting the inputs to display each state was the most time consuming.

**PART 3. SPECIAL STATE MACHINE DESIGN****Description:**

Design a solution for a sequence detector. Create a state diagram before starting to write Verilog code.

**Problem Description:**

The sequence that needs to be replicated is as follows: 0 1 1 0 1 1 0 1 0. The input is called A, where the Moore output is active on the last “0” of the sequence. The Mealy output goes active when the state machine is in the state before the Moore output goes active.

 
**Engineering Data:**

Figure 8. State Machine Diagram for the Sequence

 


Figure 9. Waveform Diagram of State Machine

```

module Part3(clk,x,y,w,current_state);

input wire x,clk;
output reg [1:0] y;
output wire w;

output reg [3:0] current_state;
reg [3:0] next_state;

parameter s0 = 4'b0000,
           s1 = 4'b0001,
           s2 = 4'b0010,
           s3 = 4'b0011,
           s4 = 4'b0100,
           s5 = 4'b0101,
           s6 = 4'b0110,
           s7 = 4'b0111,
           s8 = 4'b1000,
           s9 = 4'b1001,
           s10 = 4'b1010,
           s11 = 4'b1011,
           s12 = 4'b1100,
           s13 = 4'b1101,
           s14 = 4'b1110,
           s15 = 4'b1111;

always@(posedge clk) begin
    current_state <= next_state;
end

assign w = (current_state == s9);
always@(*) begin
    case(current_state)
        s0: if(x) begin
                    next_state <= s0;
                    y = 1;
                end
            else if (!x) begin
                    next_state <= s1;
                    y = 0;
                end
    end

    s1: if(x) begin
            next_state <= s2;
            y = 0;
        end
        else if (!x) begin
            next_state <= s0;
            y = 0;
        end
    s2: if(x) begin
            next_state <= s3;
            y = 0;
        end
        else if (!x) begin
            next_state <= s0;
            y = 0;
        end
    s3: if(x) begin
            next_state <= s0;
            y = 0;
        end
        else if (!x) begin
            next_state <= s4;
            y = 0;
        end
    s4: if(x) begin
            next_state <= s5;
            y = 0;
        end
        else if (!x) begin
            next_state <= s0;
            y = 0;
        end
    s5: if(x) begin
            next_state <= s6;
            y = 0;
        end
        else if (!x) begin
            next_state <= s0;
            y = 0;
        end
    s6: if(x) begin
            next_state <= s0;
            y = 0;
        end
        else if (!x) begin
            next_state <= s7;
            y = 0;
        end
    end
end

```

```
s7: if(x) begin
    next_state <= s8;
    y = 0;
end
else if (!x) begin
    next_state <= s0;
    y = 0;
end
s8: if(x) begin
    next_state <= s0;
    y = 1;
end
else if (!x) begin
    next_state <= s9;
    y = 0;
end
s9: if(x) begin
    next_state <= s0;
    y = 0;
end
else if (!x) begin
    next_state <= s1;
    y = 0;
end
default:
    next_state <= s0;
endcase
end
endmodule
```

**Figure 10. Verilog Code of Sequential Detector in Behavioral Modeling**

### **Conclusion:**

In conclusion when creating this I drew inspiration from the previous section because the testbench for it was similar to this part. In the end there were only nine states however there must 15 states in the parameter because we need to use four D Flip-Flops. This part took me about 45 minutes to complete. However at the end I came to understand the meaning of Mealy and Moore outputs and how they play a role in State Machines.